

ISTANBUL TECHNICAL UNIVERSITY
COMPUTER ENGINEERING DEPARTMENT

BLG 242E
DIGITAL CIRCUITS LABORATORY
EXPERIMENT REPORT

HOMEWORK NO : 3
EXPERIMENT DATE : 22.05.2022
LAB SESSION : FRIDAY - 14.00
GROUP NO : G8

GROUP MEMBERS:

150180089 : Harun Çifci
150200705 : Helin Aslı Aksoy

SPRING 2021

Contents

FRONT COVER

CONTENTS

1	INTRODUCTION [10 points]	1
2	MATERIALS AND METHODS [40 points]	1
2.1	Part 1	1
2.2	Part 2	2
2.3	Part 3	3
2.4	Part 4	4
3	RESULTS [15 points]	4
3.1	Part 1	4
3.2	Part 2	7
3.3	Part 3	9
4	DISCUSSION [25 points]	12
5	CONCLUSION [10 points]	13

1 INTRODUCTION [10 points]

In this experiment we are asked to implement three important cryptography applications in the history of cryptography. First we have implemented Caesar Cipher named after Roman Republic general and dictator Julius Caesar. Caesar Cipher was one of the first examples of cryptography in history. Julius Caesar used this encryption technique to communicate with his generals during war. The second technique we are asked to implement was Vigenere Cipher used by Confederate Army. Unlike Caesar Cipher, the Vigenere Cipher encrypts messages using a key. Both parties, the sender and receiver must have the same key for conducting communication. Finally we are asked to implement Enigma machine used by German Army in the World War 2 and we are asked to realize a sample communication environment. The Enigma machine was used to encrypt and decrypt secret messages. According to experts, the defeat of the German Army was accelerated by 2 years thanks to the work of Ultra group, which deciphered the Enigma and other encryption machines.

2 MATERIALS AND METHODS [40 points]

2.1 Part 1

In this part we have designed 4 helper modules. Detailed information is given below.

- CharDecoder Module: It transforms ASCII codes to decoded binary character. It takes 8-bit input which is the ASCII code, gives 26-bit output as decoded char.
 - char (8-bit input): ASCII code of the character.
 - decodedChar (26-bit output): Decoded output of the character.
- CharEncoder Module: It transforms the binary decoded version of the char to ASCII code. It takes 26-bit input, gives 8-bit output.
 - decodedChar (26-bit input): Decoded input of the character.
 - char (8-bit output): ASCII code of the character.
- CircularRightShift Module: It takes 26-bit input data and 5-bit shiftAmount input, gives 26-bit output. The output is data shifted to the right 'shiftAmount' times.
 - data (26-bit input): Input data.
 - shiftAmount (5-bit input): Shift amount.
 - out (26-bit output): Data shifted to the right 'shiftAmount' times.

- CircularLeftShift Module: It takes 26-bit input data and 5-bit shiftAmount input, gives 26-bit output. The output is data shifted to the left ‘shiftAmount’ times.
 - data (26-bit input): Input Data.
 - shiftAmount (5-bit input): Shift amount.
 - out (26-bit output): Data shifted to the left ‘shiftAmount’ times

2.2 Part 2

In this part, we have implemented Caesar Cipher Encryption and Decryption modules. Then we have created a Caesar Module to show encrypted and decrypted messages. Figure 1 shows the encryption technique of Caesar Cipher when the shift count is 3.

 


Figure 1: Caesar Encryption

- CaesarEncryption Module: It works like a shifter and encrypt the char using Caesar Cipher technique.
- CaesarDecryption Module: It works like a shifter and decrypt the encrypted char using Caesar Cipher technique.
- CaesarEnvironment Module: It is a module that contains CaesarEncryption and CaesarDecryption modules inside.

To implement these modules we have used helper modules that we have implemented at the previous part. The abstract diagram of the Caesar Encryption and Decryption Process is as follows.

 


Figure 2: Caesar Encryption

2.3 Part 3

In this part, we have implemented the Vigenere Cipher Encryption and Decryption modules. Then, we have created a Vigenere Module to show encrypted and decrypted messages. Vigenere Cipher uses the same key message for encryption and decryption processes. Equation 1 and Equation 2 show encryption and decryption calculations of the Vigenere Cipher, respectively. Vigenere Cipher's key message is "KADIROZLEM" and the plain text is "ISTANBULTECHNICAL".

$$C_i = (P_i + K_i) \mod 26$$

Figure 3: Cipher Char Equation

where C_i is the cipher char, P_i is the plain char, and K_i is the key char.

$$D_i = (C_i - K_i) \mod 26$$

Figure 4: Decrypted Char Equation

where D_i is the decrypted char, C_i is the cipher char, and K_i is the key char.

The modules that we have implemented for the Vigenere Cipher as given below.

- **VigenereEncryption Module:** It encrypts the char using Vigenere Cipher technique. It has 2 char input, one of them is plain char which is going to be encrypted. The other one is key char. It has 1 bit clock and load input that allows registers to work. It gives 8-bit encrypted char output.
- **VigenereDecryption Module:** It decrypts the char using Vigenere Cipher technique. It has 2 char input, one of them is plain char which is encrypted. The other one is key char. It has 1 bit clock and load input that allows registers to work. It gives 8-bit decrypted char output.

- VigenereEnvironment Module: It is a module that contains VigenereEncryption and VigenereDecryption modules inside.

2.4 Part 4

In this part, we have tried to implement the Enigma machine. The Enigma machine can both encrypt and decrypt a message. For secure communication, receiver and transmitter must have Enigma machines which are configured and initiated identically. The rotors in the Enigma machine rotate every time a new input character is given and this rotation changes the configuration of the machine entirely. This way, a character is decrypted differently every time it is given as an input.

3 RESULTS [15 points]

3.1 Part 1

```

1 module CharDecoder_simulation();
2     reg [7:0] char;
3     wire [25:0] decodedChar;
4
5     CharDecoder uut(char, decodedChar);
6
7     initial
8     begin
9         char = 8'd90; #142.85;
10        char = 8'd66; #142.85;
11        char = 8'd67; #142.85;
12        char = 8'd68; #142.85;
13        char = 8'd69; #142.85;
14        char = 8'd70; #142.85;
15        char = 8'd71; #142.85;
16    end
17
18 endmodule

```

Listing 1: CharDecoder Module

 


Figure 5: CharDecoder Simulation

```

1 module CharEncoder_simulation();
2     reg [25:0] decodedChar;
3     wire [7:0] char;
4
5     CharEncoder uut(decodedChar, char);
6
7     initial
8     begin
9         decodedChar = 26'b10000000000000000000000000000000; #142.85;
10        decodedChar = 26'b00000000000000000000000000000010; #142.85;
11        decodedChar = 26'b00000000000000000000000000000100; #142.85;
12        decodedChar = 26'b000000000000000000000000000001000; #142.85;
13        decodedChar = 26'b0000000000000000000000000000010000; #142.85;
14        decodedChar = 26'b00000000000000000000000000000100000; #142.85;
15        decodedChar = 26'b000000000000000000000000000001000000; #142.85;
16    end
17
18 endmodule

```

Listing 2: CharEncoder Module

 


Figure 6: CharEncoder Simulation

```

1 module CircularLeftShiftSimulation();
2     reg [25:0] data;
3     reg [4:0] shiftAmount;
4     wire [25:0] out;
5     CircularLeftShift uut(shiftAmount, data, out);
6
7     initial begin

```

```

8      data = 26'b10000000000000000000000000; shiftAmount = 5'b00001;
      #250;
9      data = 26'b01000000000000000000000000; shiftAmount = 5'b00001;
      #250;
10     data = 26'b00100000000000000000000000; shiftAmount = 5'b00001;
      #250;
11     data = 26'b00010000000000000000000000; shiftAmount = 5'b00001;
      #250;
12     end
13 endmodule

```

Listing 3: LeftShift Module

 


Figure 7: CircularLeftShift Module Simulation

```

1 module CircularRightShiftSimulation();
2     reg [25:0] data;
3     reg [4:0] shiftAmount;
4     wire [25:0] out;
5     CircularRightShift uut(shiftAmount, data, out);
6
7     initial begin
8         data = 26'b10000000000000000000000000; shiftAmount = 5'b00001;
9         #250;
10        data = 26'b01000000000000000000000000; shiftAmount = 5'b00001;
11        #250;
12        data = 26'b00100000000000000000000000; shiftAmount = 5'b00001;
13        #250;
14        data = 26'b00010000000000000000000000; shiftAmount = 5'b00001;
15        #250;
16    end
17 endmodule

```

Listing 4: RightShift Module

 


Figure 8: CircularRightShift Module Simulation

3.2 Part 2

```

1 module CaesarCipherEncryption_simulation();
2     reg [7:0] plainChar;
3     reg [4:0] shiftCount;
4     wire [7:0] chipherChar;
5
6     CaesarCipherEncryption uut(plainChar, shiftCount, chipherChar);
7
8     initial
9     begin
10         plainChar = 8'd72; shiftCount = 0; #200;
11         plainChar = 8'd65; shiftCount = 4; #200;
12         plainChar = 8'd82; shiftCount = 20; #200;
13         plainChar = 8'd85; shiftCount = 14; #200;
14         plainChar = 8'd78; shiftCount = 0; #200;
15     end
16
17 endmodule

```

Listing 5: Decryption Module

 


Figure 9: CaesarCipherEncryption Module Simulation

```

1 module CaesarCipherDecryption_simulation();
2     reg [7:0] chipherChar;
3     reg [4:0] shiftCount;
4     wire [7:0] decryptedChar;
5
6     CaesarCipherDecryption uut(chipherChar, shiftCount, decryptedChar);

```

```

7
8  initial
9  begin
10     chipherChar = 8'd72; shiftCount = 0; #200;
11     chipherChar = 8'd69; shiftCount = 4; #200;
12     chipherChar = 8'd76; shiftCount = 20; #200;
13     chipherChar = 8'd73; shiftCount = 14; #200;
14     chipherChar = 8'd78; shiftCount = 0; #200;
15  end
16
17 endmodule

```

Listing 6: Encryption Module

 


Figure 10: CaesarCipherDecryption Module Simulation

```

1 module CaesarEnvironment_simulation();
2     reg [7:0] plainChar;
3     reg [4:0] shiftCount;
4     wire [7:0] chipherChar;
5     wire [7:0] decryptedChar;
6
7     CaesarEnvironment uut(plainChar, shiftCount, chipherChar,
8         decryptedChar);
9
10    initial
11    begin
12        plainChar = 8'd75; shiftCount = 3; #200;
13        plainChar = 8'd65; shiftCount = 1; #200;
14        plainChar = 8'd68; shiftCount = 15; #200;
15        plainChar = 8'd73; shiftCount = 4; #200;
16        plainChar = 8'd82; shiftCount = 3; #200;
17    end
18 endmodule

```

Listing 7: Environment Module

 


Figure 11: CaesarEnvironment Module Simulation

3.3 Part 3

```

1 module Vigenere_Cipher_Decryption_simulation();
2     reg [7:0] chipherChar;
3     reg [79:0] keyInput;
4     reg load;
5     reg CLK;
6     wire [7:0] decryptedChar;
7     Vigenere_Cipher_Decryption uut(chipherChar, keyInput, load, CLK,
8     decryptedChar);
9
10    initial begin
11        CLK = 0; load = 1; chipherChar = "O"; keyInput = "KADIROZLEM";
12        #100;
13        load = 0; chipherChar = "R"; #100;
14        load = 0; chipherChar = "L"; #100;
15        load = 0; chipherChar = "S"; #100;
16        load = 0; chipherChar = "P"; #100;
17        load = 0; chipherChar = "S"; #100;
18        load = 0; chipherChar = "Q"; #100;
19        load = 0; chipherChar = "T"; #100;
20        load = 0; chipherChar = "Q"; #100;
21        load = 0; chipherChar = "Y"; #100;
22    end
23
24    always begin
25        CLK <= ~CLK; #50;
26    end
27 endmodule

```

Listing 8: Decryption Module

 


Figure 12: Vigenere Decryption Simulation

```

1 module Vigenere_Cipher_Encryption_simulation();
2     reg [7:0] plainChar;
3     reg [79:0] keyInput;
4     reg L;
5     reg Clock;
6     wire [7:0] chipherChar;
7     Vigenere_Cipher_Encryption uut(plainChar, keyInput, L, Clock,
8         chipherChar);
9
10    initial begin
11        Clock = 0; L = 1; plainChar = "E"; keyInput = "KADIROZLE"; #100;
12        L = 0; plainChar = "R"; #100;
13        L = 0; plainChar = "I"; #100;
14        L = 0; plainChar = "K"; #100;
15        L = 0; plainChar = "Y"; #100;
16        L = 0; plainChar = "E"; #100;
17        L = 0; plainChar = "R"; #100;
18        L = 0; plainChar = "I"; #100;
19        L = 0; plainChar = "M"; #100;
20        L = 0; plainChar = "M"; #100;
21    end
22
23    always begin
24        Clock <= ~Clock; #50;
25    end
26
27 endmodule

```

Listing 9: Encryption Module

 


Figure 13: Vigenere Encryption Simulation

```

1 module VigenereEnvironment_simulation();
2     reg [7:0] plainChar;
3     reg [79:0] keyInput;
4     reg load;
5     reg CLK;
6     reg CLK2;
7     wire [7:0] chipherChar;
8     wire [7:0] decryptedChar;
9     VigenereEnvironment_Module uut(plainChar, keyInput, load, CLK, CLK2 ,
10     chipherChar, decryptedChar);
11
12     initial begin
13         CLK = 0; CLK2 = 0; load = 1; plainChar = "P"; keyInput = "
14         DIGITALLAB"; #100;
15         load = 0; plainChar = "A"; #100;
16         load = 0; plainChar = "L"; #100;
17         load = 0; plainChar = "Y"; #100;
18         load = 0; plainChar = "A"; #100;
19         load = 0; plainChar = "C"; #100;
20         load = 0; plainChar = "O"; #100;
21         load = 0; plainChar = "L"; #100;
22         load = 0; plainChar = "U"; #100;
23         load = 0; plainChar = "K"; #100;
24
25     end
26
27     always begin
28         CLK <= ~CLK; #50;
29     end
30
31     always begin
32         #0.4
33         CLK2 <= ~CLK2; #49.6;
34     end
35 end

```

Listing 10: Environment Module

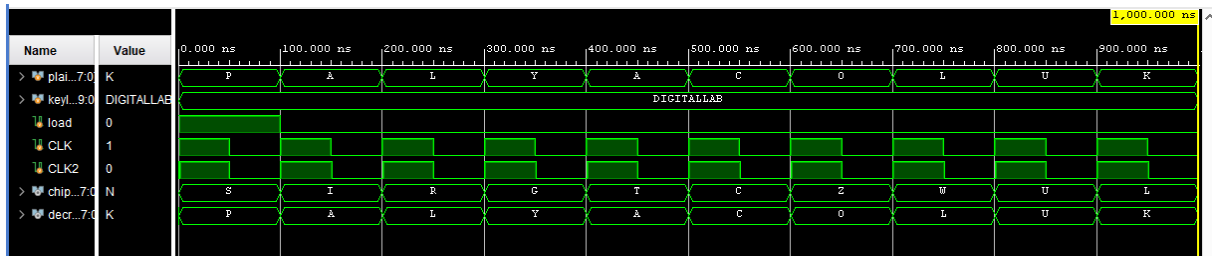


Figure 14: Vigenere Environment Simulation

4 DISCUSSION [25 points]

In the first part of experiment, we are asked to build some helper modules for part 2 such as; encoder, decoder, right shifter and left shifter. Encoder transforms ASCII to encoded binary char. Decoder works vice versa. Shifters are used to map the characters to another character as Caesar Method works like that.

In the second part of experiment, we have implemented Caesar Cipher with the help of modules we have created in previous part. We have implemented 3 modules in this part such as: Caesar Encryption, Caesar Decryption and Caesar Environment. In Caesar Encryption module, we have 2 inputs plainChar and shiftCount and 1 output chipherChar. First, we have used Decoder module and decode plainChar input. Then, we have used Right Shift module and shift our decoded char to right. Lastly, we have encoded our decoded char with Encoder module. Caesar Decryption module has the same structure with Caesar Encryption module but instead of shifting right between decoder and encoder we are shifting to left. In the Caesar Environment we have used Encryption and Decryption Modules. We have taken a plainChar and shiftCound as input and gave chipherChar and decryptedChar output.

In the third part, We have implemented Vigenere Module. Vigenere Cipher uses the same key message for encryption and decryption processes. We have implemented 3 modules: Vigenere Encryption, Vigenere Decryption and Vigenere Environment. In Vigenere Encryption module, we have taken 4 inputs plainChar, keyInput, LOAD and CLK and gave output chipherChar. We have used " $C_i = (P_i + K_i) \bmod 26$ " equation to calculate chipherChar if LOAD is 0. If LOAD is 1, it loads the keyInput into keyRegister. Vigenere Decryption module has same structure with Encryption but it uses a different equation to calculate decryptedChar, " $D_i = (C_i - K_i) \bmod 26$ ". In Vigenere Environment we have used both Encryption and Decryption modules consecutively and we have taken

4 inputs such as Load, CLK, plainChar and keyInput and gave 2 outputs, chipherChar and decryptedChar.

5 CONCLUSION [10 points]

Since it is an interesting working area we have thought about the topic and made some searches on it. We have learned many different Cryptology methods other than Caesar, Vigenere. Also story of Enigma and it's connection with computer engineering was impressive. Unfortunately, due to lack of time we could not make the Enigma but we have learned workflow of it.